2 cards on 2 readers to open 1 Door

APPLICATION NOTE
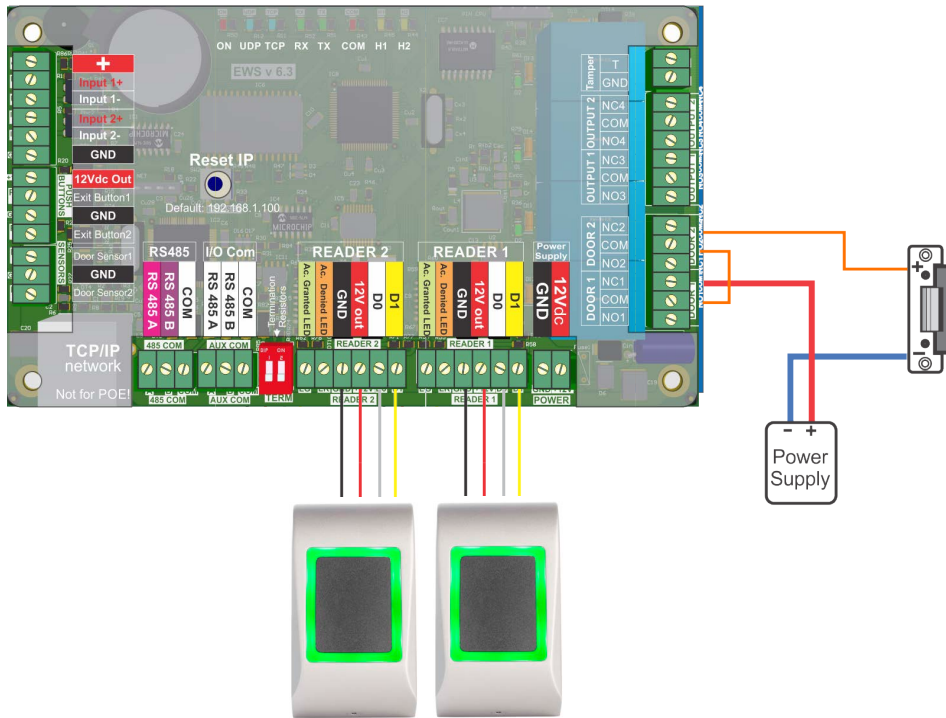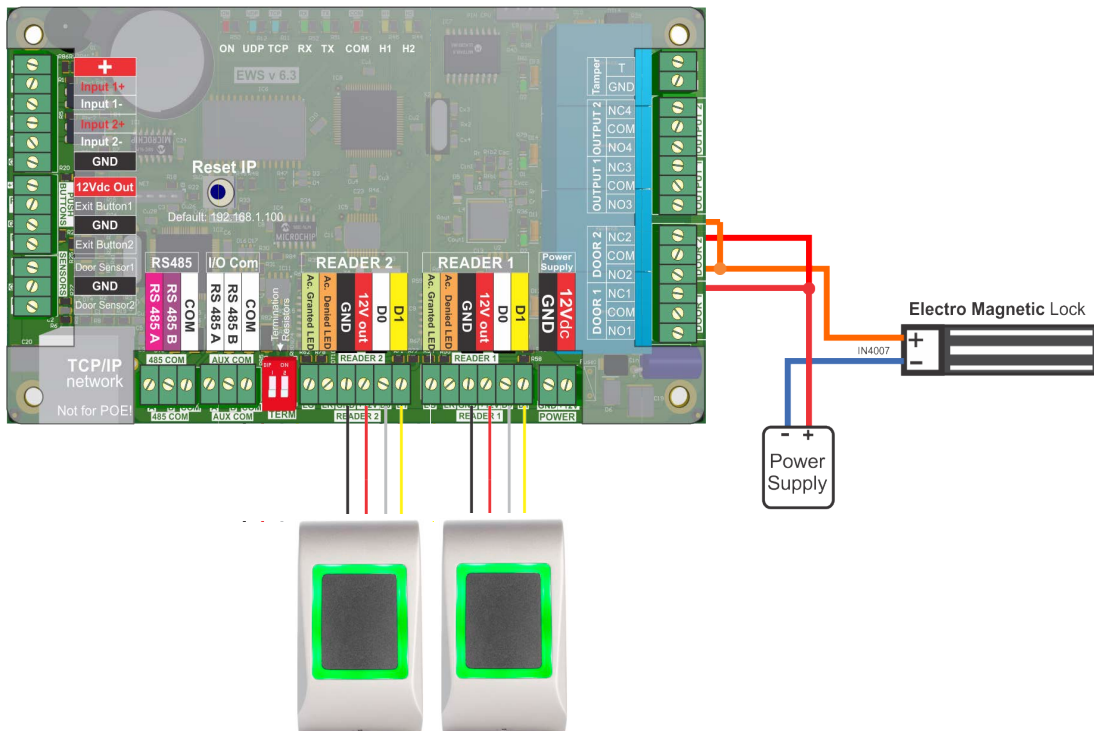
If Strike is used connect the relays in series

If Magnet is used connect the relays in parallel

v.b1

1. Create 2 Access levels. First ONLY for Door1, second only for Door2.
2. Assign that Access levels to 2 different Cards.
3. use those 2 cards to open the door.

All product specifications are subject to change without notice.